

## How to use a SCART TV as a Monitor for MAME

As the title suggests this is guide to connecting a PC to a TV via it's SCART (aka Peritel or Euroconnector) socket. Specifically, for use with the arcade game emulator [AdvanceMame](#) (a port of [MAME](#) specially for arcade monitors and TVs) though the info is just as valid for other applications.

There's not a lot of difference between a TV and an arcade monitor. A TV can be thought of as an arcade monitor + a TV tuner + an audio amplifier in a plastic box. To use a TV as an arcade monitor the TV must provide inputs for RGB video which comes out of arcade boards, computers, etc. Here's where the SCART input comes in, not only does it accept RGB video (0.7Vp-p @ 75ohms, same as a computer monitor) it also has a couple of handy control lines. There are TVs with RGB inputs that use something other than a SCART input but they are quite rare. SCART sockets are often found on TVs found in Europe/Australia. Sometimes a TV can have more than one SCART input, usually one socket accepts Luma/Chroma (S-Video) and the other RGB video.

Note: Much of this information is not applicable to arcade monitors. Please see the [Arcade Monitor Interface Circuits](#) page if that's what you're after.

[More info + pinouts for the SCART connector](#)

### The Circuit/Cable...


#### Fixing the Sync

In order for the TV to accept video from the PC we must first:

1. Run special software (AdvanceMame in this case) the PC to reduce horizontal scan rate from ~31khz to ~15khz
2. Combine horizontal and vertical sync signals to make 'composite video sync' (0.3v/75 ohms).
3. Take the CVBS status line high (10-12v) to enable input from pin 20 (composite video)
4. Take the RGB status line high (1-3v) to enable input from pins 7, 11 and 15 (RGB)

Some (expensive) TVs can automatically switch the status lines themselves when a signal is present but most don't. Also some TVs will switch CVBS on with only 5v on the CVBS Status line but the majority need the full 12 volts.


Here are two circuits for combining the sync signals...

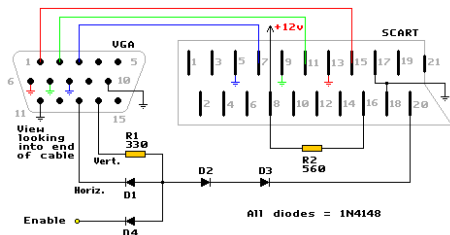**Dodgy Diode VGA to SCART circuit**

Horizontal and vertical sync signals must be negative for the circuit to function (this is the default for AdvanceMame).

This circuit ANDs the two sync signals together using diode logic. The H and V sync signals from the video card need to be able to source/sink a reasonable amount of current for this circuit to operate properly. This isn't a problem for every modern video card I've come across but may be for older (ISA) cards. Pin 11 of the VGA connector is connected to ground to tell the computer that a colour 'monitor' is connected (sometimes this pin is already wired to ground inside the connector).

The Enable input is to facilitate shutting down (kill) the sync during boot (more info [down the page](#)). If this feature isn't required then D4 can be omitted.

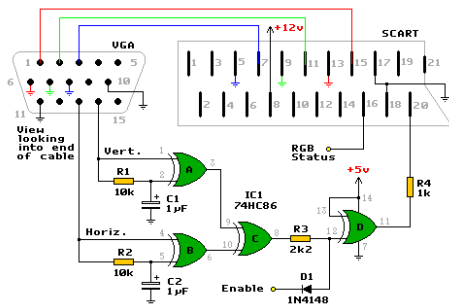**Enhanced VGA to SCART circuit (with Enable)**

This circuit will adjust to any sync polarity making it much more versatile than the 'Dodgy Diode' circuit. It also XORs the two sync signals instead of just ANDing them. If a TV has problems syncing to the

output of the simple circuit this might resolve them.

C1, R1, IC1A and C2, R2, IC1B are there to adjust the polarity to to the input of IC1C. IC1C is to XOR the two sync signals together to make composite sync. IC1D inverts the composite sync which is output through a resistor (to drop the voltage to 0.3Vp-p) into the composite sync input.

[Here](#) is a version without an enable input.


## Protecting The TV During Boot

During boot the video signals from the PC will be at a frequency too high for the TV to handle. Feeding the TV these signals will cause it to lose sync and produce an unstable/rolling/duplicated image. Aside from being annoying it can, in some cases, cause damage to the TV. To prevent the wrong signals reaching the TV, an Enable input has been added to both VGA > SCART circuits. This allows the sync to be disabled during boot (or any other time the H. frequency is too high). There's also a RGB Status input to the SCART socket which will blank the screen when off. This is usually turned off with the Enable line to stop out of sync video appearing on the screen.

Input	Off	On	Impedance
RGB Status	0-0.4V, disable video (RGB) input	1-3V, enable video (RGB) input	75 ohms
Enable	0-0.4V, disable sync	>4V or floating, enable sync	-


Here are four circuits that can be used to manipulate these inputs...

### Manual Switch

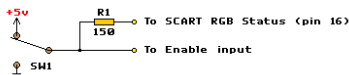

Very simple, just a switch (and a resistor to drop the voltage for the RGB Status pin). It's not very practical but is useful for testing. Make sure switch is of the break before make variety.
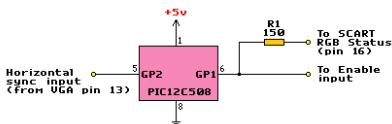
### Automatic Enable Circuit I (using a PIC microcontroller)




The PIC requires programming, see resources for programmers/software.

[Binary](#) - all you need to program the chip (.hex)

[Source](#) - the asm source code

This is the ideal Enable circuit. The Horizontal sync line is monitored by the PIC, any time it goes higher than ~17khz the Enable line is pulled low along with the RGB Status line (video muting).
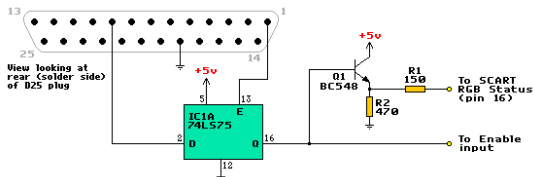
### Automatic Enable Circuit II (using the PC's Parallel Port)




**Equivalents...** A 74HC75 or 74AC75 should work if a 74LS75 isn't available (if a HC or AC is used all unused inputs must be connected to Vdd(+5v) or Ground). Any general purpose NPN transistor (2N2222, 2N3904, PN100, etc) will work in place of Q1.

For anyone unable to program a PIC or just wants more control over the TV. The Enable/RGB Status line is controlled by data bit 7 on the parallel port.

The popular emulator front end, ArcadeOS, can toggle this bit automatically on startup. All that is required is adding a line in the config file. If another front end is going to be used then download AdvanceCAB. It contains some very useful utilities, notably AdvanceVGA and AdvancePORTIO. AdvanceVGA is used to change the video mode to one that will display on the TV and AdvancePORTIO is used to write to the parallel port. In the autoexec.bat you would put something like...

```
vga /c pal.rc          ::sets the video mode
portio 378 80         ::sets data bit 7. 80h = 128 decimal.
portio 37A 1          ::pulse strobe line to load-
portio 37A 0          :: data into the latch register
```
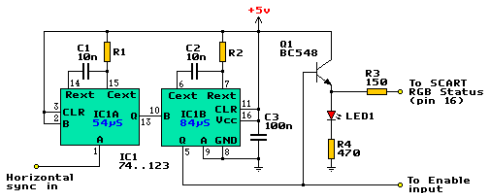
### Automatic Enable Circuit III (with the 74xx123)



This circuit works like 'Auto Enable I' in that it detects when the sync goes over a certain frequency ( $18.5\text{kHz} \pm 10\%$ ). The circuit consists of two retriggerable one shots. On each horizontal sync pulse IC1A is triggered and generates a  $54\mu\text{s}$  pulse. If H-sync is  $\sim 15\text{kHz}$  then the  $54\mu\text{s}$  pulse will trigger IC1B every  $64\mu\text{s}$ . As IC1B is set for an  $84\mu\text{s}$ , the pulse coming in every  $64\mu\text{s}$  constantly retriggers it, keeping the output (Q) at a logic high. If H-sync rises above  $\sim 18.5\text{kHz}$  the time between each sync pulse drops below  $54\mu\text{s}$  and IC1A is retriggered constantly. The output from IC1A is just a logic high and as there are no pulses to trigger IC1B it's output is a logic low.


Bastard manufactures! It seems there's no standard 74xx123 out there, many of them use a slightly different 'K' value in their timing formula. The formula is  $T_w = R * C * K$  ( $T_w$  in seconds,  $R$  in ohms,  $C$  in farads). Check the table below for different  $K$  values along with suggested  $R1/R2$  values for different parts. If the resistor value is non-standard then series/parallel multiple resistors to get close, within 5% is fine.

PART	MANUFACTURER	K	R1	R2
SN74LS123	Texas Instruments	0.33	16k	25k
HD74LS123	Hitachi	0.38	14k	22k
DM74LS123	Fairchild Semiconductor	0.4	13.5k	21k
SN74LS123	Motorola	0.45	12k	18k
74HC123	Philips	0.45	12k	18k
CD74HC123	Texas Instruments	0.45	12k	18k
M74HC123	ST Microelectronics	0.45	12k	18k
M74HC123A	ST Microelectronics	1	5.5k	8.2k
MM74HC123	Fairchild Semiconductor	1	5.5k	8.2k
MM74HC123	National Semiconductor	1	5.5k	8.2k

The LED is there for easy testing (you can make sure it's working before plugging hooking it to a TV).

## Audio

SCART audio input with volume control

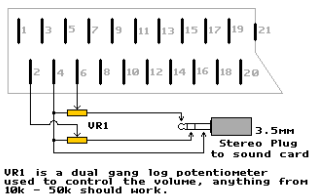


Make use of the (usually) stereo amplifier in the TV. For the volume control to work properly the volume on the TV and sound card should be turned up to their maximum (or loudest you want the volume to go).
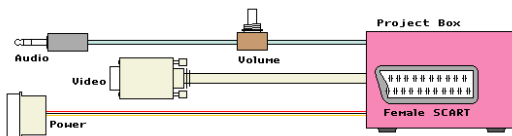
## Construction

First a thing to do is find a cable with a VGA (HD15) connector already attached, a cable hacked off an old monitor or a VGA cable (cut off one end) is perfect. Sometimes there's enough room inside the connectors to build the circuit, ie the simple circuit can be wired point to point inside the SCART socket and the Parallel Port Enable circuit will easily fit into a D25 shell.

If more space is required then build the circuit on a piece of veroboard or prototype board and mount it inside a small project box. Mount a female SCART connector on the side and drill a hole for the cables to poke through. Something like...



A standard SCART cable has some wires crossed over so make sure you take that into account if wiring to a female connector.

#### Standard SCART Cable Wiring

Audio Output Right	1	1	Audio Output Right
Audio Input Right	2	2	Audio Input Right
Audio Output Left	3	3	Audio Output Left
Audio Ground	4	4	Audio Ground
Blue Ground	5	5	Blue Ground
Audio Input Left	6	6	Audio Input Left
Blue Video	7	7	Blue Video
CVBS Status	8	8	CVBS Status
Green Ground	9	9	Green Ground
Data D2B inverted	10	10	Data D2B inverted
Green Video	11	11	Green Video
Data D2B	12	12	Data D2B
Red Ground	13	13	Red Ground
Data D2B Ground	14	14	Data D2B Ground
Red Video	15	15	Red Video
RGB Status	16	16	RGB Status
CVBS Ground	17	17	CVBS Ground
Status Ground	18	18	Status Ground
CVBS Output	19	19	CVBS Output
CVBS Input	20	20	CVBS Input
Shield Ground	21	21	Shield Ground

CVBS = Composite of Video, Blanking and Sync  
often shortened to 'Composite Video'

Grounding is pretty straight-forward. Connect each colour's ground to the appropriate SCART pin and connect the VGA's ground wire (pin 10) to any one of the SCART's ground connections (pins 17, 18 or 21). You could connect it to all three if you like but it isn't necessary.

## Testing

For a quick test to see if the circuit is working properly run [vgatv](#) at the DOS prompt (not windows). Remember to use the /isp (invert sync polarity) switch if testing the simple circuit.

## For the Experienced/Brave



I've designed a PCB for the Enhanced VGA -> SCART + the PIC based Enable circuit small enough to fit into the space inside a SCART plug. It uses mostly surface mount components to achieve it's small size. C1 and C2 are tantalum type capacitors and there is an additional decoupling capacitor mounted between

the power and ground pins of the PIC.

[PCB Layout](#) - Print at 600dpi

[PCB Layout](#) - in Protel Autotrax format

[PCB Component Overlay](#)

[Photo 1](#) - Solder side (bigger version of image above)

[Photo 2](#) - Other side

## Other stuff...

Once the VGA to SCART cable has been constructed there are a few other adjustments that may need to be made to the TV.

## Adjusting Overscan



Overscan is where the image is scanned beyond the boundaries of the screen. TV manufacturers do this to eliminate the possibility of black borders and non-video information appearing on the screen. Typical overscan is 5 - 10% which is a bit too much for an arcade-monitor-like usage.

On older TV sets the overscan can be reduced by adjusting the Horizontal/Vertical height controls located inside the set. To make this adjustment on newer TVs, enter service mode and make the required adjustments with the remote control via the on screen display. Info on making these adjustments can be found in the TV's service manual (you'll probably have to rent/buy one).

## Power


In a MAME cabinet it's desirable to have TV come on when power is applied. Does the TV have a...

Mains power switch - This type is most ideally suited to a MAME cabinet, simply switch it on and it will come on every time you apply power.

Soft power switch - These switches are much smaller than the mains type and have much less travel. When power is applied to these TVs they tend to go into 'standby' mode, to avoid this, wire a jumper over the power switch (usually a tactile type).

No power switch - These TVs are designed to be turned on and off via the remote control and do away with a power switch all together. Like the soft power TVs, these ones usually go into standby mode when power is applied. The way to get it out of standby mode is by pressing one of the program (channel) +/- buttons. Unfortunately, simply wiring a jumper over one of the program buttons won't work because the TV will constantly change channel (brings up an annoying OSD). A circuit to get around the problem....

TV automatic power circuit

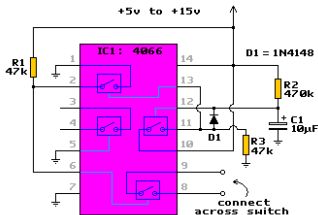

What this circuit does is close the switch for ~3 seconds when power is applied. The amount of time the switch is closed for can be varied by changing the value of R2. The formula is  $T = R2 * C1 * 0.7$  (ie.  $470 * 10^3 * 10 * 10^{-6} * 0.7 = 3.29$  seconds). This circuit should be powered by the TV itself. Find a 5-15v power rail that's active while the TV is in standby mode, if the remote sensor can be located then there's usually a +5v rail going to one of it's pins. If a suitable source of power can't be found inside the TV then (after making sure the TV doesn't have a hot chassis) hook it up to the 12v supply from the PC.

Modifying a TV like this requires a basic knowledge of how TVs work and the associated dangers lurking inside. Unplug and let the TV sit for a while before working on it.

## Resources

### Information

[SCART pinouts and information](#)

[GamesX's video primer](#)

[Tomi Engdahl's VGA to TV information centre](#)

[Build Your Own Arcade Controls](#)

### Software

[Advance Projects](#) - home of AdvanceMAME, AdvanceMenu and more.

[PC2IAMMA](#) - home of ArcadeOS and Vantage (I wonder if this works on a TV..)

[EnTech's Powerstrip](#)

[VGATV](#)

[SciTech Display Doctor and UNIVBE](#) - both are now free to download.

[Mon-ARC](#) - another vga > 15khz TSR

[Raine](#) - Another multi arcade game emulator (faster than MAME in most cases).

[← BACK TO INDEX](#)

### Changelog

**1/9/06** - Fixed automatic enable circuit III again....this circuit really does work now.

**30/12/05** - Modified automatic enable circuit III - now based on an 74LS123.

**26/8/05** - Finally started a changelog :). I found out the other day that my 'Simple...' was very poor and didn't function properly (and nobody told me!). It's now been replaced with the Dodgy Diode circuit which really does work. Apologies to anyone who built the Simple... circuit. Also added in this update is a fourth Enable circuit.



-----  
**17/4/05** - Fixed/added something???

**\*\*/\*\*/04** - Rewrote the page.

**\*\*/12/03** - Page Created

Tim Worthington, email: eviltim at optusnet.com.au

